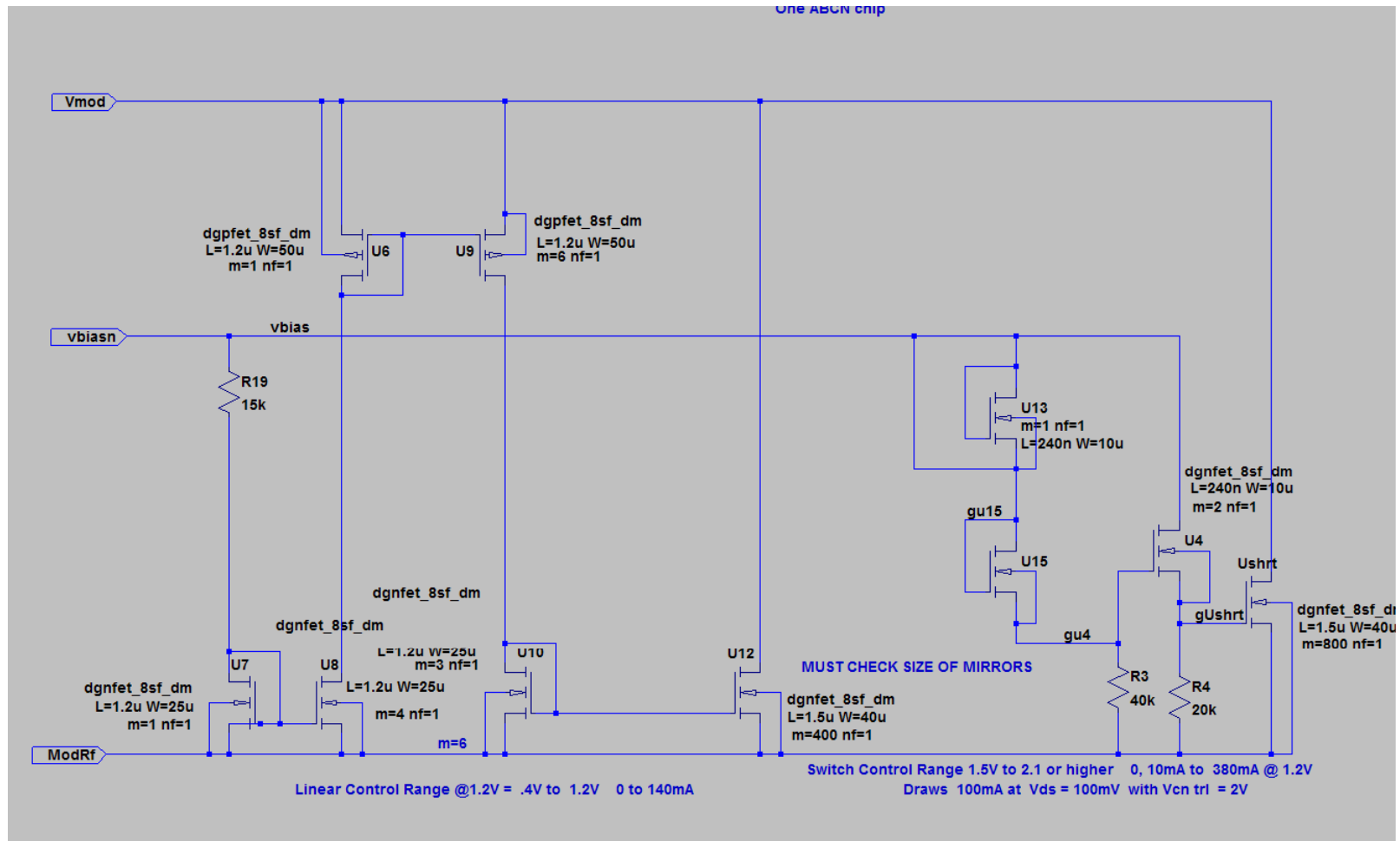


Slave Shunt for ABCn 130nm

February 2010


Mitch and Nandor

Shunt Slave for 130nm Designs




DC Simulations


Vary Control Current

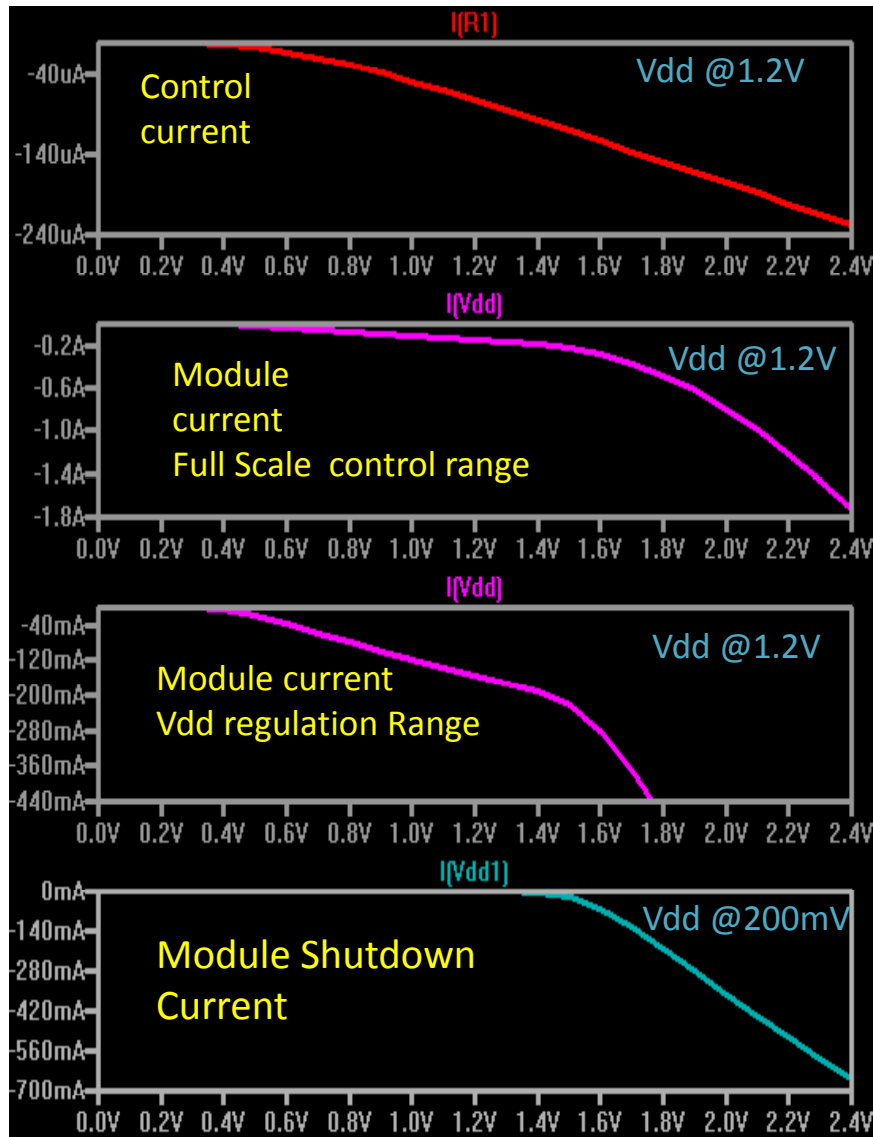

Control Voltage

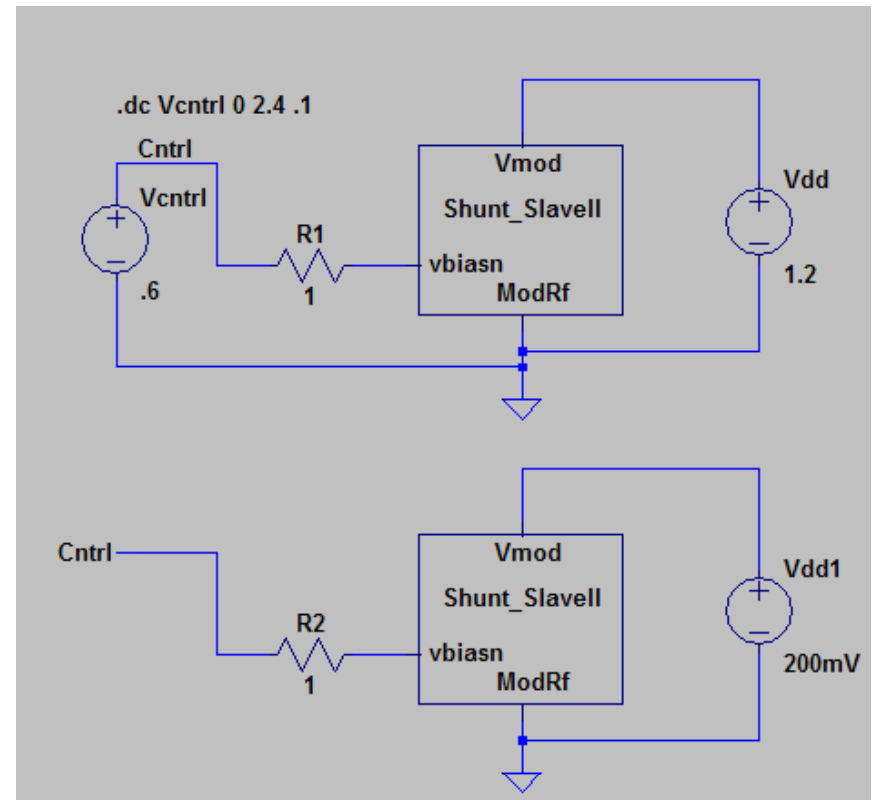

Shunt Response Time

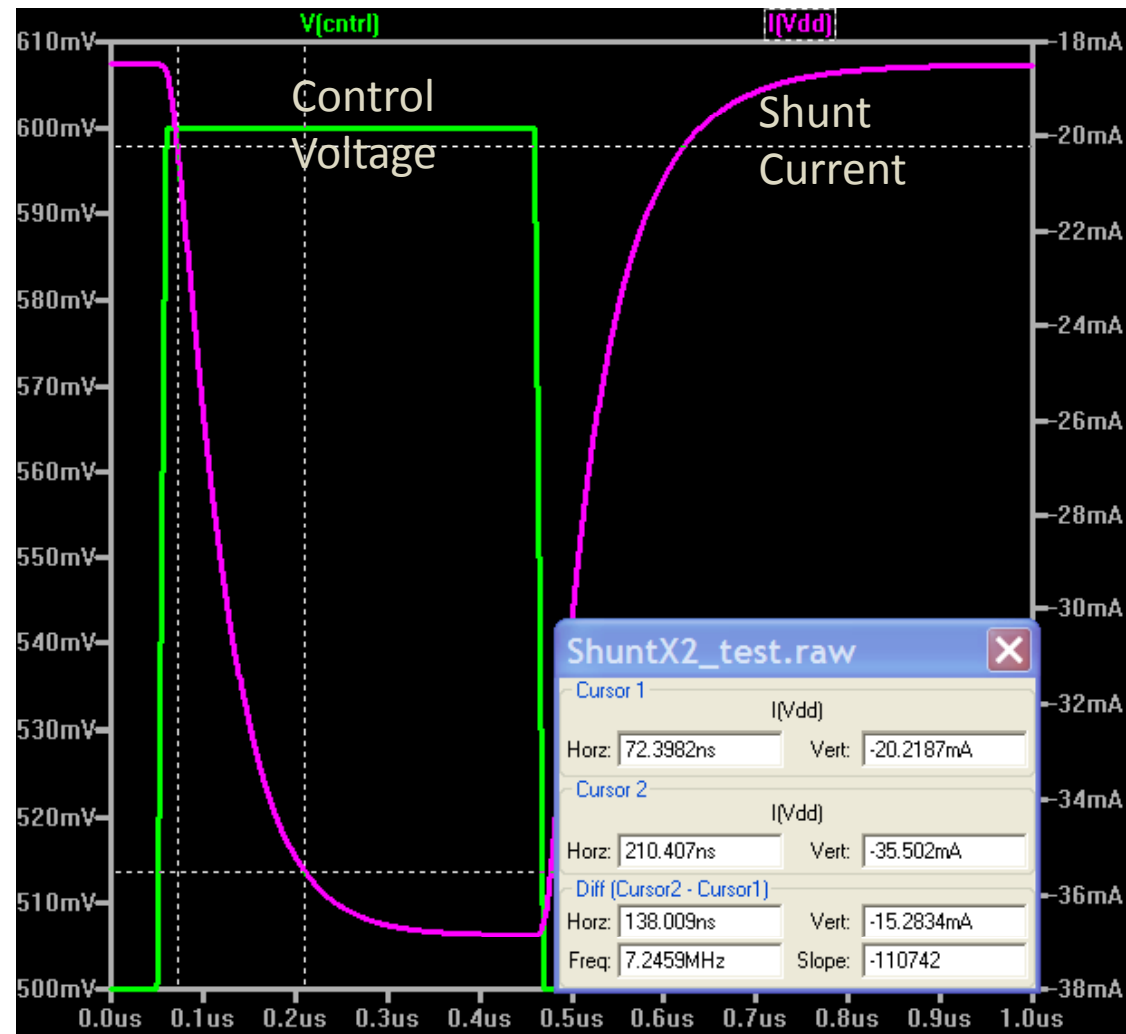

Status Feb 1

Schematic Simulations done

Needs to be put into Cadence Layout